

## FINAL-EIN 13 – Electrical Installer Theory Examination Marking Schedule

Notes: 1. (1 mark) means that the preceding statement/answer earns 1 mark.

2. This schedule sets out the accepted answers to the examination questions. A marker can exercise their discretion and decide on the overall accuracy of any answer that is presented in the candidate's own words.

3. Symbols and terms - alternatives

Power                      W or P

Voltage                  V or E or U

Phase                    Active

Question 1	<i>Reference Marks</i>	<i>Marking notes</i>
(a) $R_2 = \frac{R_1 \times L_1}{L_2}$ $= \frac{100 \times 100}{300}$ $= 33.33 \text{ M}\Omega$	(½ mark)  (½ mark)  (1 mark)	
(b) This test voltage is used to avoid destroying or damaging the semi-conductor components.	(2 marks)	
(c) $\text{pf} = \frac{P}{\sqrt{3} \times V \times I}$ $= \frac{40000}{\sqrt{3} \times 405 \times 63.5}$ $= 0.898 \text{ lag}$	(½ mark)  (½ mark)  (1 mark)	
(d) • It ensures that the voltage never rises above 230 V under fault conditions. • It ensures that the potential difference between neutral and the general mass of earth will always be about 0V.	(1 mark)  (1 mark)	
(e) (i) $1\text{M}\Omega$  (ii) $0.01\text{M}\Omega$	(1 mark)  (1 mark)	
(f) There is an internal volt drop due to the impedance of the windings.	(2 marks)	
(g) Better mechanical protection.	(2 marks)	
(h) To ensure that the minimum sized mains cable can be selected.	(2 marks)	

<b>Question 1</b>	<i>Reference Marks</i>	<i>Marking notes</i>
(i) The protective device must be capable of safely clearing that level of prospective short-circuit current without damage.	(2 marks)	
(j) The power output of the heater will drop.	(2 marks)	

Question 2	Marks	Reference	Marking notes
<p>(a) (i) To provide a warning where turning on the point of isolation would cause personal danger.</p> <p>(ii) A danger tag is attached to a point of isolation of electrical equipment being worked on.</p> <p>(iii) Any THREE of:</p> <ul style="list-style-type: none"> <li>• Ensure the correct isolating switch is selected.</li> <li>• Ensure the isolating switch is in the OFF position.</li> <li>• Each person concerned must fasten a tag to the isolation switch.</li> <li>• Danger tags must be securely fastened.</li> </ul> <p>(iv) • Where each electrical installer has finished work.</p> <ul style="list-style-type: none"> <li>• Where an authorised person is satisfied that it is safe to remove the tags.</li> </ul>	<p>(1 mark)</p> <p>(1 mark)</p> <p>(3 marks)</p> <p>(2 marks)</p>		
<p>(b) • An out-of-service tag is attached to faulty or damaged electrical equipment.</p> <ul style="list-style-type: none"> <li>• To warn against reconnection where use of the equipment would cause more damage or could cause injury.</li> </ul>	<p>(1 mark)</p> <p>(1 mark)</p>		
<p>(c) Any ONE of:</p> <ul style="list-style-type: none"> <li>• Test between each phase and earth.</li> <li>• Test between each phase and neutral.</li> </ul>	<p>(1 mark)</p>		

Question 3	Marks	Reference	Marking notes
<p>(a) (i) • It shows that the higher the fault current</p> <p>• The lower the time it takes the fuse to trip.</p> <p>(ii) • With a 50A fault current flowing in the 16A fuse will blow in 2.8 s.</p> <p>• With a 100A fault current flowing in the 16A fuse will blow in 0.1 s.</p> <p>(iii) 20 x 1.5 = 30A</p> <p>(iv) 95A</p>	<p>(1 mark)</p> <p>(1 mark)</p> <p>(1 mark)</p> <p>(1 mark)</p> <p>(½ mark)</p> <p>(½ mark)</p> <p>(1 mark)</p>		
<p>(b) Correct discrimination occurs when only the protective device protecting the final subcircuit operates.</p>	<p>(2 marks)</p>		
<p>(c) • To provide short-circuit protection for the circuit and motor.</p> <p>• Because the thermal overloads are not designed for this type of protection.</p>	<p>(1 mark)</p> <p>(1 mark)</p>		

Question 4	Marks	Reference	Marking notes
<p>(a) (i) <math>I_{PH} = \frac{V_{PH}}{R_{PH}}</math>  <math>= \frac{230}{26.45}</math>  <math>I_{PH} (I_L) = 8.7A</math></p> <p>(ii) <math>P = \sqrt{3} \times V_L \times I_L \times pf</math>  <math>= \sqrt{3} \times 400 \times 8.7 \times 1</math>  <math>= 6027.36 W</math></p> <p>(iii) <math>1.5 \text{ mm}^2</math></p> <p>(iv) <math>10A</math></p>	<p>(½ mark)</p> <p>(½ mark)</p> <p>(1 mark)</p> <p>(½ mark)</p> <p>(½ mark)</p> <p>(1 mark)</p> <p>(½ mark)</p> <p>(½ mark)</p>		
<p>(b) (i) <math>I_{PH} = \frac{V_{PH}}{R_{PH}}</math>  <math>= \frac{400}{26.45}</math>  <math>= 15.12A</math>  <math>I_L = I_{PH} \times \sqrt{3}</math>  <math>= 15.12 \times \sqrt{3}</math>  <math>= 26.2A</math></p> <p>(ii) <math>P = \sqrt{3} \times V_L \times I_L \times pf</math>  <math>= \sqrt{3} \times 400 \times 26.2 \times 1</math>  <math>= 18151.36W</math></p>	<p>(½ mark)</p> <p>(1 mark)</p> <p>(½ mark)</p> <p>(½ mark)</p> <p>(1 mark)</p> <p>(½ mark)</p> <p>(1 mark)</p>		


**Question 5**

Marks


Reference

Marking notes

(a)

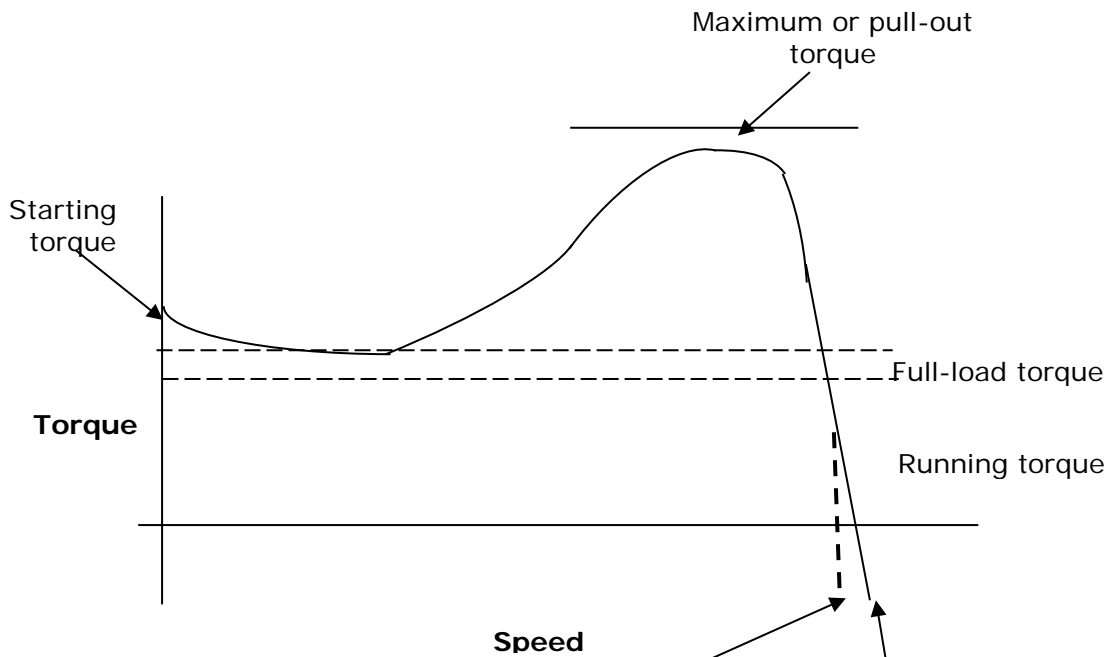

- The starting torque (½ mark)
- The pull-out torque (½ mark)
- Full-load torque (½ mark)
- Running torque (½ mark)
- Rotor speed –  $N_R$  (½ mark)
- Synchronous speed  $N_S$ . (½ mark)

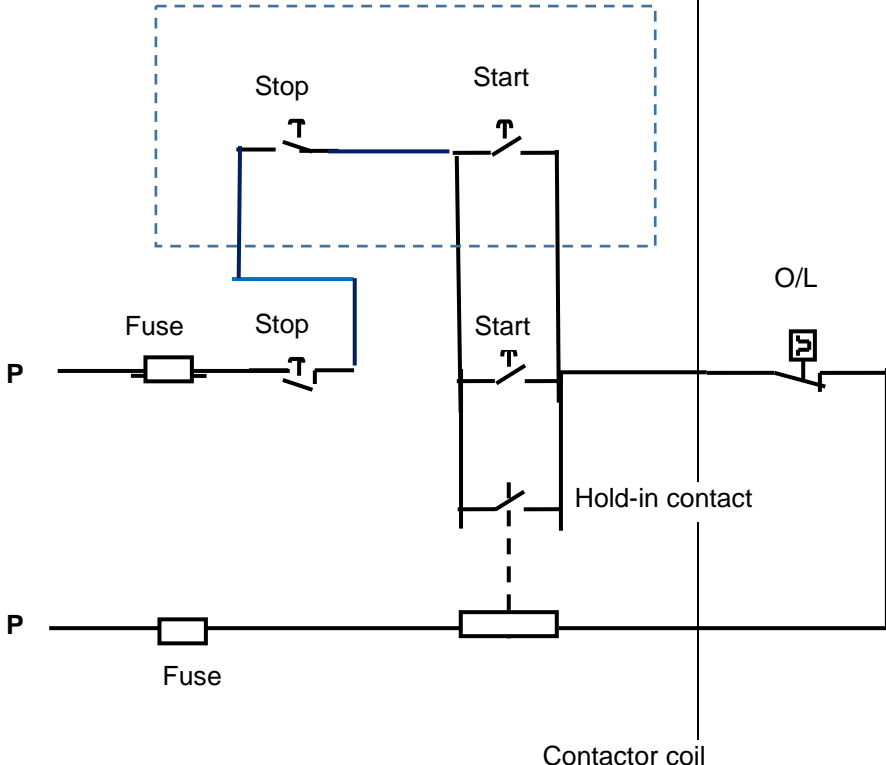Question 5	Marks	Reference	Marking notes
<p>(b)</p>  <p>(i)</p> <ul style="list-style-type: none"> <li>• Correctly connected fuses (1 mark)</li> <li>• Correctly connected start button (½ mark)</li> <li>• Correctly connected stop button (½ mark)</li> <li>• Correctly connected hold-in contact (½ mark)</li> <li>• Correctly connected coil (½ mark)</li> <li>• Correctly connected thermal overload (½ mark)</li> <li>• Working circuit (½ mark)</li> </ul> <p>(ii)</p> <ul style="list-style-type: none"> <li>• The remote stop is in series with the local stop button (1 mark)</li> <li>• The remote start in parallel with the local start button (1 mark)</li> <li>• There is no link between the stop and the start buttons in the starter (1 mark)</li> </ul>			

Question 6	Reference Marks	Marking notes
(a) $pf = \cos\Phi$ $= \cos 35^\circ$ $= 0.8191 \text{ lag}$	(½ mark)  (½ mark)	
(b) Input power = $\frac{\text{Output power}}{\text{Efficiency}}$ $= \frac{4000}{0.83}$ $= 4819.27 \text{ W}$	(½ mark) (½ mark) (1 mark)	
(c) $I_L = \frac{P_{\text{Input}}}{\sqrt{3} \times V_L \times pf}$ $= \frac{4819.27}{\sqrt{3} \times 400 \times 0.8191}$ $= 8.5 \text{ A}$	(½ mark) (½ mark) (1 mark)	
(d) (i) $N = \frac{60f}{P}$ $= \frac{60 \times 60}{2}$ $= 1800 \text{ rpm}$  Slip speed = $N \times \text{slip}$ $= 1800 \times 4\%$ $= 72 \text{ rpm}$  (ii) Rotor speed = $N - \text{slip speed}$ $= 1800 - 72$ $= 1728 \text{ rpm}$	(½ mark) (½ mark) (½ mark)  (½ mark) (½ mark) (½ mark)  (½ mark) (½ mark) (1 mark)	



Question 7	Marks	Reference	Marking notes
(a) Any THREE of: <ul style="list-style-type: none"> <li>• The trip mechanism is operational.</li> <li>• The PRCD trips at its rated residual current in the required time.</li> <li>• The PRCD trips when voltage ceases to be supplied.</li> <li>• The PRCD remains tripped when electricity supply is restored.</li> </ul>	(3 marks)		
(b) Any TWO of: <ul style="list-style-type: none"> <li>• Install RCD at the switchboard at the origin of the final subcircuit.</li> <li>• Install an SRCD on the bathroom socket outlet.</li> <li>• Install an SRCD on a socket outlet upstream from the new socket outlet in the bathroom.</li> </ul>	(2 marks)		
(c) <ul style="list-style-type: none"> <li>• Overcurrent</li> <li>• Short circuit</li> <li>• Earth leakage</li> </ul>	(½ mark) (½ mark) (½ mark)		
(d) (i) 30 milliamps.  (ii) 10 milliamps  (iii) 300 milliamps.	(½ mark)  (½ mark)  (½ mark)		
(e) <ul style="list-style-type: none"> <li>• No.</li> <li>• It does not operate on residual pulsating direct current.</li> </ul>	(1 mark) (1 mark)		

Question 8	Reference Marks	Marking notes
(a) <ul style="list-style-type: none"> <li>• Voltage</li> <li>• Frequency</li> </ul>	(1 mark) (1 mark)	
(b) <ul style="list-style-type: none"> <li>A Rectifier</li> <li>B Smoothing circuit (d.c. link)</li> <li>C Any ONE of: <ul style="list-style-type: none"> <li>• Inverter</li> <li>• d.c. to a.c. Converter</li> </ul> </li> <li>D Control unit</li> </ul>	(½ mark) (½ mark) (½ mark)  (½ mark)	
(c) Changes the three-phase a.c. supply to a d.c. supply.	(1 mark)	
(d) Changes the d.c. supply back to a three-phase a.c. supply	(1 mark)	
(e) <ul style="list-style-type: none"> <li>• The motor would overheat.</li> <li>• As there would be minimal fan cooling at low speed.</li> </ul>	(1 mark) (1 mark)	
(f) Any TWO of: <ul style="list-style-type: none"> <li>• Easier to control the starting current</li> <li>• Easier to control the starting torque</li> <li>• Multiple variations of the time it takes from rest to full speed (or full-load torque).</li> <li>• Reduces mechanical shock to equipment</li> <li>• More even torque</li> <li>• Reduces disruption to supply voltage</li> </ul>	(2 marks)	

Question 9	Reference Marks	Marking notes
(a) A Main winding B Centrifugal switch C Start capacitor D Rotor E Run capacitor F Auxilliary winding	(½ mark) (½ mark) (½ mark) (½ mark) (½ mark) (½ mark)	
(b) (i) By an external current relay  (ii) 60% to 80% of full-load speed	(1 mark)  (1 mark)	
(c) Any ONE of: <ul style="list-style-type: none"> <li>• It runs a lot quieter</li> <li>• It develops a higher running torque</li> <li>• It develops a higher starting torque</li> </ul>	(2 marks)	
(d) VA = 235 x 14.7 = 3454.5 VA  Pf = $\frac{W}{VA}$ = $\frac{3000}{3454.5}$ = 0.87	(½ mark) (½ mark)  (½ mark) (½ mark) (1 mark)	